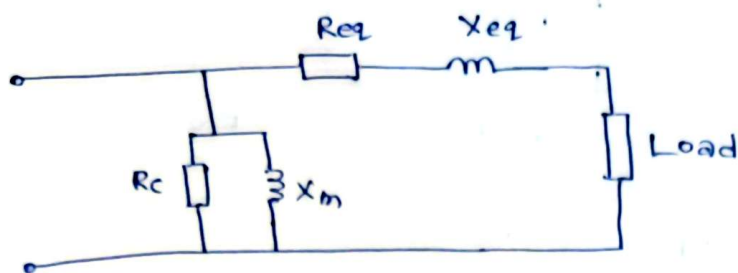


255: ELECTRIC POWER


NGLE PHASE TRANSFORMER

21/345 Samarakoon S.M.O.T.



- $R_c \rightarrow$ core loss resistance. Represent losses in the core
- $X_m \rightarrow$ magnetization reactance. Represent the magnetizing current needed to establish flux in the core.
- $R_{eq} \rightarrow$ this is equivalent leakage resistance. This is because primary and secondary sides have some leakage flux in a practical transformer.
- $X_{eq} \rightarrow$ both flux losses in primary and secondary are transformed to the winding as X_{eq} .

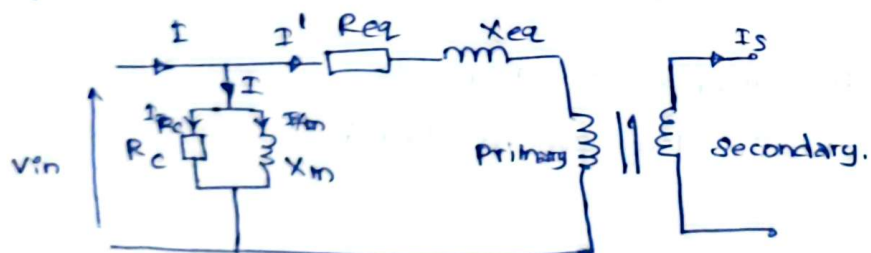Open circuit test is used to obtain X_m & R_c .



The secondary side is O.C.!

$$I_s = 0$$

$$I' = 0$$

$$N = \frac{V_{out}}{V_{in}}$$

$$P_n = \frac{V_{in}^2}{R_c}$$

$$\Phi = VI \sin \theta$$


$$I_{Xm} = I_{in} - I_{Rc}$$

$$I_{Xm} = \sqrt{I_{in}^2 - I_{Rc}^2}$$

$$X_m = \frac{|V_{in}|}{|I_{Xm}|}$$

$$I_{Rc} = \frac{V_{in}}{R_c}, R_c = \frac{V_{in}^2}{P_n}$$


$$P = VI \cos \theta$$

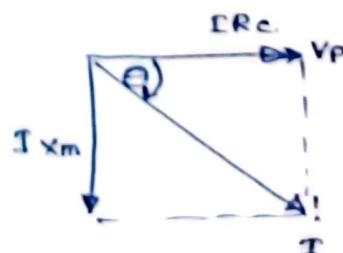

$$\theta = \cos^{-1}(P/n)$$


* Open circuit test is used to measure X_m and R_c .

⑦

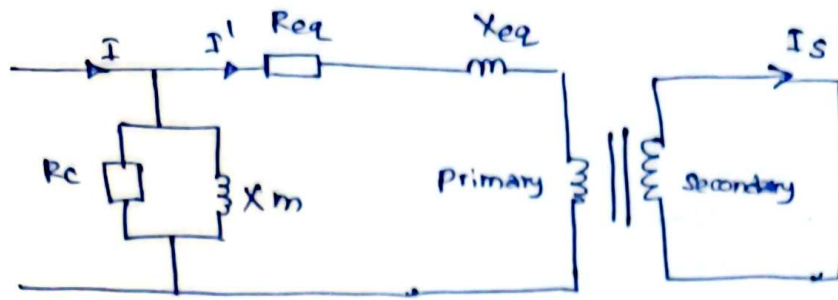

* short circuit test used to obtain R_{eq} & X_{eq} .

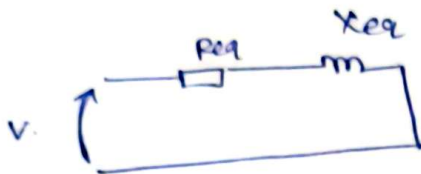Give $\frac{1}{10} \times V_{rated}$ as the input voltage.




$$P_{sc} = I_{sc}^2 R_{eq}$$

$$R_{eq} = \frac{P_{sc}}{I_{sc}^2}$$

$$Z_{eq} = \frac{V}{I}$$

$$X_{eq} = \sqrt{Z_{eq}^2 - R_{eq}^2}$$

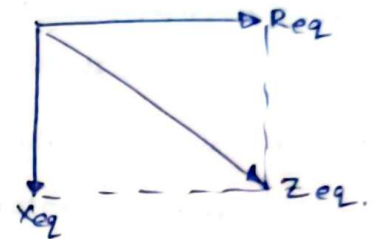

$$R_{eq} = \frac{P_{sc}}{I_{sc}^2}$$

$$\sqrt{P_{sc}} = \sqrt{R_{eq}} \cdot I_{sc}$$

\uparrow \uparrow \uparrow
 y m x

from the gradient of graph of $\sqrt{P_{sc}}$ Vs I_{sc} , R_{eq} can be found.