

TABULATION

Table 08: Observation data for the earth electrode test

Length (m)	Resistance (Ω)
0	1.2
1.5	1.8
3.0	1.9
4.5	2.5
6.0	3.0
7.5	3.5
9.0	4.0
10.5	4.5
12.0	6.0
13.5	9.5
15.0	200

CALCULATIONS

Resistances of different sizes of wires at 20 °C are:

$$1 \text{ mm}^2 = 18 \text{ m}\Omega/\text{m}$$

$$1.5 \text{ mm}^2 = 12 \text{ m}\Omega/\text{m}$$

$$2.5 \text{ mm}^2 = 7 \text{ m}\Omega/\text{m}$$

Inside the building is 30 °C:

$$R_t = [1 + 0.004(t-20)] \times R_{20}$$

Resistances of different sizes of wires at 30 °C are:

$$1 \text{ mm}^2 \text{ wire; } R_{30} = [1 + 0.004(30-20)] \times 18 \text{ m}\Omega/\text{m}$$

$$R_{30} = 18.72 \text{ m}\Omega/\text{m}$$

$$1.5 \text{ mm}^2 \text{ wire; } R_{30} = [1 + 0.004(30-20)] \times 12 \text{ m}\Omega/\text{m}$$

$$R_{30} = 12.48 \text{ m}\Omega/\text{m}$$

$$2.5 \text{ mm}^2 \text{ wire; } R_{30} = [1 + 0.004(30-20)] \times 7 \text{ m}\Omega/\text{m}$$

$$R_{30} = 7.28 \text{ m}\Omega/\text{m}$$

Part 2.1

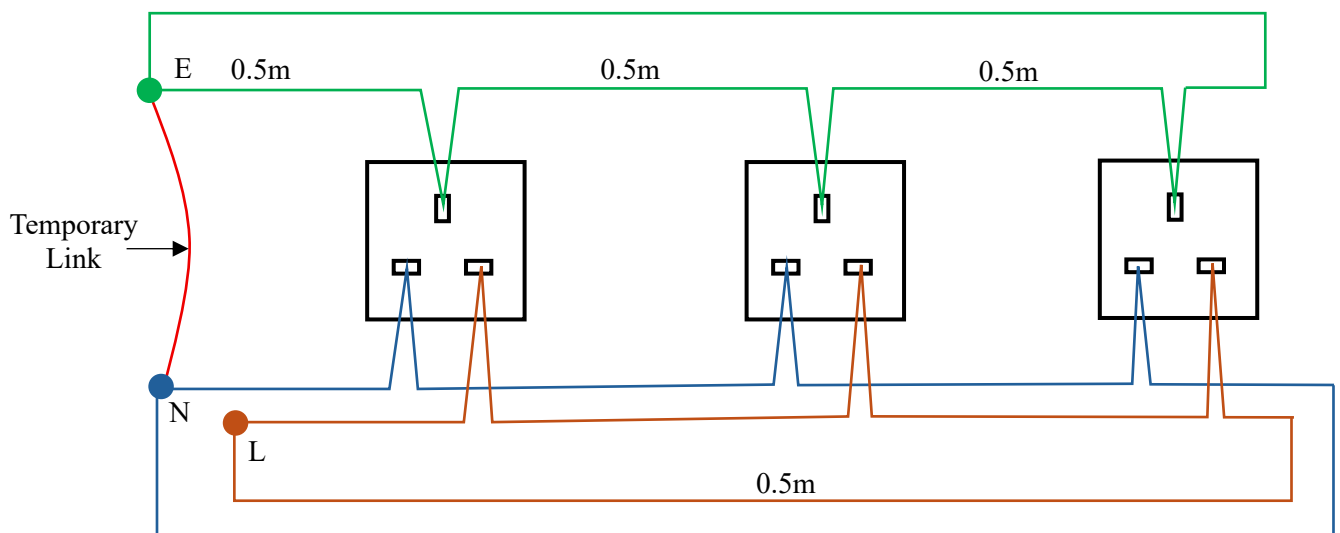


Figure 05 : Circuit 2 with a temporary link between neutral and earth

Since all wires are 2.5mm² and 0.5 m ;

$$R_L = R_N = R_E = 7.28 \text{ m}\Omega/\text{m} \times 0.5 \text{ m}$$

$$= 3.64 \text{ m}\Omega$$

Resistance between earth(E) and neutral(N);

$$\begin{aligned}
 \text{At the socket outlet 1} \quad &= (R_N + R_E) // (3 \times R_N + 3 \times R_E) \\
 &= 2 \times 3.64 \text{ m}\Omega // 6 \times 3.64 \text{ m}\Omega \\
 &= \frac{6}{(3+1)} \times 3.64 \text{ m}\Omega \\
 &= \underline{\underline{5.46 \text{ m}\Omega}}
 \end{aligned}$$

$$\begin{aligned}
 \text{At the socket outlet 2} \quad &= (2 \times R_N + 2 \times R_E) // (2 \times R_N + 2 \times R_E) \\
 &= 4 \times 3.64 \text{ m}\Omega // 4 \times 3.64 \text{ m}\Omega \\
 &= \frac{4 \times 4}{(4+4)} \times 3.64 \text{ m}\Omega \\
 &= \underline{\underline{7.28 \text{ m}\Omega}}
 \end{aligned}$$

$$\begin{aligned}
 \text{At the socket outlet 3} \quad &= (3 \times R_N + 3 \times R_E) // (R_N + R_E) \\
 &= 6 \times 3.64 \text{ m}\Omega // 2 \times 3.64 \text{ m}\Omega \\
 &= \frac{6}{(3+1)} \times 3.64 \text{ m}\Omega \\
 &= \underline{\underline{5.46 \text{ m}\Omega}}
 \end{aligned}$$

Part 2.2

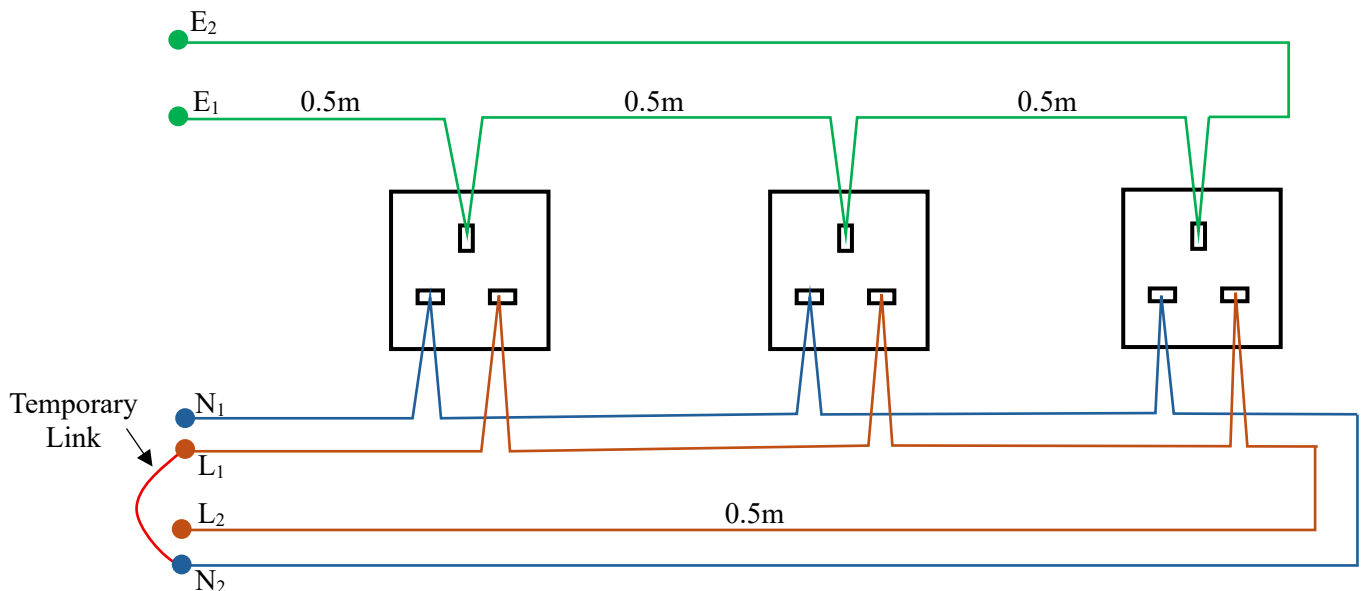


Figure 06 : Disconnected circuit 2 with a temporary link between L₁ and N₂

$$\begin{aligned}
 \text{Resistance between N}_1 \text{ and L}_2 \quad &= 4 \times R_N + 4 \times R_L \\
 &= 8 \times 3.64 \text{ m}\Omega \\
 &= \underline{\underline{29.12 \text{ m}\Omega}}
 \end{aligned}$$

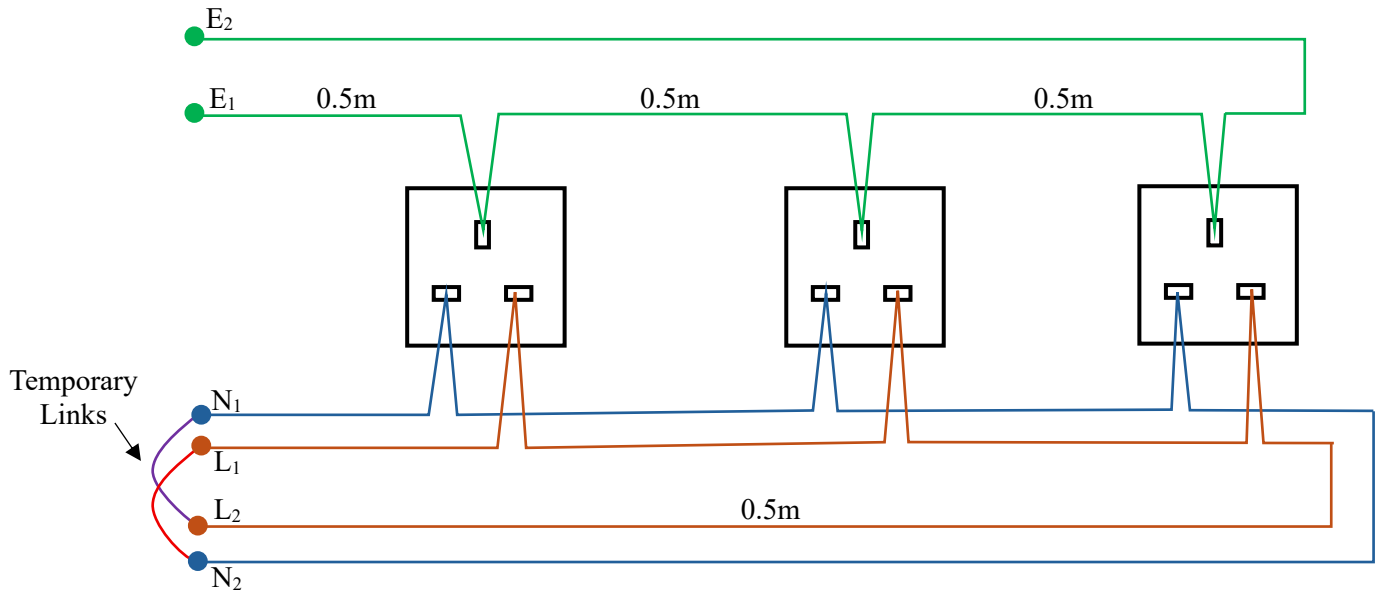


Figure 07 : Disconnected circuit 2 with temporary links between L_1 N_2 and L_2 N_1

Resistance between live(L) and neutral(N);

At the socket outlet 1

$$\begin{aligned}
 &= (1 \times R_L + 3 \times R_N) // (1 \times R_N + 3 \times R_L) \\
 &= 4 \times 3.64 \text{ m}\Omega // 4 \times 3.64 \text{ m}\Omega \\
 &= \frac{4 \times 4}{(4+4)} \times 3.64 \text{ m}\Omega \\
 &= \underline{\underline{7.28 \text{ m}\Omega}}
 \end{aligned}$$

At the socket outlet 2

$$\begin{aligned}
 &= (2 \times R_L + 2 \times R_N) // (2 \times R_N + 2 \times R_L) \\
 &= 4 \times 3.64 \text{ m}\Omega // 4 \times 3.64 \text{ m}\Omega \\
 &= \frac{4 \times 4}{(4+4)} \times 3.64 \text{ m}\Omega \\
 &= \underline{\underline{7.28 \text{ m}\Omega}}
 \end{aligned}$$

At the socket outlet 3

$$\begin{aligned}
 &= (1 \times R_L + 3 \times R_N) // (1 \times R_N + 3 \times R_L) \\
 &= 4 \times 3.64 \text{ m}\Omega // 4 \times 3.64 \text{ m}\Omega \\
 &= \frac{4 \times 4}{(4+4)} \times 3.64 \text{ m}\Omega \\
 &= \underline{\underline{7.28 \text{ m}\Omega}}
 \end{aligned}$$

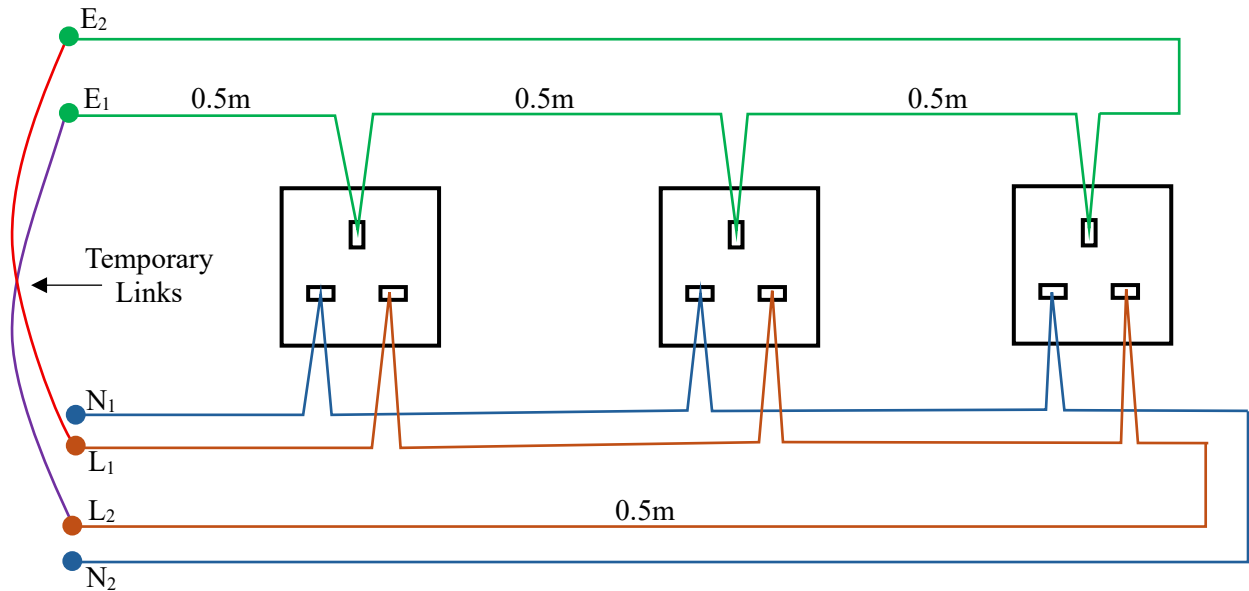


Figure 08 : Disconnected circuit 2 with temporary links between L₁ E₂ and L₂ E₁

Resistance between live(L) and earth(E);

At the socket outlet 1

$$\begin{aligned}
 &= (1 \times R_L + 3 \times R_E) // (1 \times R_E + 3 \times R_L) \\
 &= 4 \times 3.64 \text{ m}\Omega // 4 \times 3.64 \text{ m}\Omega \\
 &= \frac{4 \times 4}{(4+4)} \times 3.64 \text{ m}\Omega \\
 &= \underline{\underline{7.28 \text{ m}\Omega}}
 \end{aligned}$$

At the socket outlet 2

$$\begin{aligned}
 &= (2 \times R_L + 2 \times R_E) // (2 \times R_E + 2 \times R_L) \\
 &= 4 \times 3.64 \text{ m}\Omega // 4 \times 3.64 \text{ m}\Omega \\
 &= \frac{4 \times 4}{(4+4)} \times 3.64 \text{ m}\Omega \\
 &= \underline{\underline{7.28 \text{ m}\Omega}}
 \end{aligned}$$

At the socket outlet 3

$$\begin{aligned}
 &= (1 \times R_L + 3 \times R_E) // (1 \times R_E + 3 \times R_L) \\
 &= 4 \times 3.64 \text{ m}\Omega // 4 \times 3.64 \text{ m}\Omega \\
 &= \frac{4 \times 4}{(4+4)} \times 3.64 \text{ m}\Omega \\
 &= \underline{\underline{7.28 \text{ m}\Omega}}
 \end{aligned}$$

Part 3.1

62% of 15 m

$$= 15 \times 0.62 \text{ m} = 9.3 \text{ m}$$

Resistance at 9.3 m

$$\begin{aligned}
 &= \frac{(9.3-4.5)}{(10.5-4.5)} \times (4.5 - 2.5) + 2.5 \text{ }\Omega \text{ (considering the linear region)} \\
 &= \underline{\underline{4.1 \text{ }\Omega}}
 \end{aligned}$$

REFERENCES